

King Saud University

College of Science

Department of Mathematics

151 MATH EXERCISES

(6)

BOOLEAN ALGEBRAS

&

LOGIC GATES

&

MINIMIZATION OF CIRCUITS



Malek Zein AL-Abidin

♠1440

2018

Q2. Let B is a Boolean Algebra and $x, y \in B$. Show that $x + y = xy + xy' + x'y$ is valid.

x	y	x'	y'	xy	xy'	$x'y$	$xy + xy' + x'y$	$x + y$
1	1	0	0					
1	0	0	1					
0	1	1	0					
0	0	1	1					

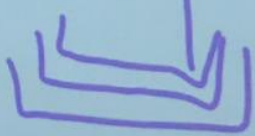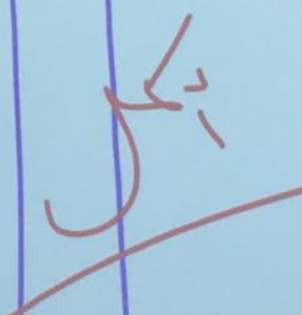

151 Math Discrete Mathematics - Boolean Algebras & Logic Gates By Malek Zein AL-Abidin
 Q5. Let $f(x, y, z) = (x' + z)(x + y)$. Find $CSP(f)$ (sum-of-products expansion) and $CPS(f)$ (product-of-sums expansion) ?

$$f = x'y + xz + yz. (Sp)$$

$$CSP(f) = xyz + xy'z + x'y'z + x'y'z'$$

$$f' = xyz' + xy'z' + x'y'z' + x'y'z$$

$$CPS(f) = (f')' = (x' + y' + z). (x' + y + z). (x + y + z). (x + y + z')$$

$yz \quad yz' \quad y'z' \quad y'z$

x	1	0	0	1
x'	1	1	0	0

151 Math Discrete Mathematics Boolean Algebras & Logic Gates By Malik Zein AL-Abidin

Q6. Let $f(x, y, z) = (x' + y)'(x + y + z) = xy'(x + y + z) = xy' + xy'z$

(5P)

(i) Use NAND gates to construct circuits with this output.

(ii) Use NOR gates to construct circuits with this output.


#6] (i) NAND

Step(1): $f = xy' + xy'z$

Step(2): $f' = (xy' + xy'z)'$

Step(3): $f = (f')' = [(xy' + xy'z)']'$

Step(4):

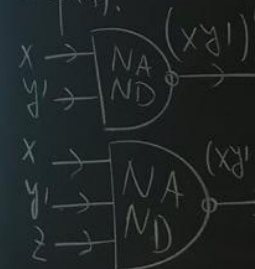

$x y' + x y' z$
 (SP)


#6] (i) NAND

Step(1): $f = x y' + x y' z$ (SP)

Step(2): $f' = (x y')' \cdot (x y' z)'$ (x)

Step(3): $f = (f')' = [(x y')' \cdot (x y' z)']'$

Step(4):

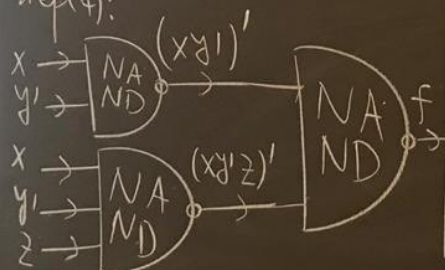


(ii) NOR

Step(1): $f' = (x' + y) \cdot (x' + y + z) = g(x, y, z)$ (PS)

Step(2): $g' = (x' + y)' + (x' + y + z)'$

Step(3): $g = (g')' = [(x' + y)' + (x' + y + z)']'$

Step(4):

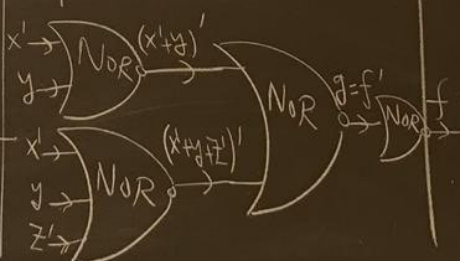

Q7. Let $f(x, y, z) = (x + y)(x' + yz')$ = $x y z' + x' y + y z'$ (SOP)

(i) Find $CSP(f)$ and $CPS(f)$.

(ii) Find $MSP(f)$ and $MPS(f)$.

(iii) Construct a minimal circuit using (AND-OR) gates, with $f(x, y, z)$ output.

Sol. $CSP(f) = x y z' + x' y z + x' y z'$

$f' = x y z + x y' z' + x y' z + x' y' z' + x' y' z$

$CPS(f) = (f')' = (x' + y' + z)' = (x' + y' + z)(x' + y' + z')(x + y + z)(x + y + z')$

	yz	$y'z$	yz'	$y'z'$
x	0	1	0	0
x'	1	1	0	0

Q7. Let $f(x, y, z) = (x+y)(x'+yz')$ $= xyz' + x'y + yz'$ (SOP)

(i) Find $CSP(f)$ and $CPS(f)$
 (ii) Find $MSP(f)$ and $MPS(f)$
 (iii) Construct a minimal circuit using (AND-OR) gates with $f(x, y, z)$ output

(ii) $MSP(f) = x'y + yz'$

$f' = y' + xz$

$MPS(f) = (f')' = y \cdot (x' + z')$

(iv) NAND
 NOR.

Truth Table for $f(x, y, z) = xyz' + x'y + yz'$:

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Handwritten notes on the screen include a Karnaugh map for f and f' , and a minimal circuit diagram.

#7]


(iv) (a) NAND

Step(1): $MSP(f) = x'y + yz'$

Step(2): $f' = (x'y)' \cdot (yz')'$

Step(3): $f = (f')' = [(x'y)' \cdot (yz')']'$

Step(4):

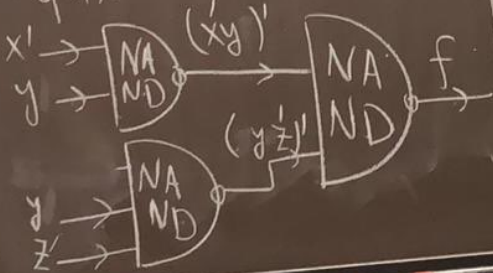


(b) NOR

Step(1): $MSP(f) = y' + (x' + z)'$


Step(2): $f' = y' + (x' + z)'$

Step(3): $f = (f')' = [y' + (x' + z)']'$

Step(4):

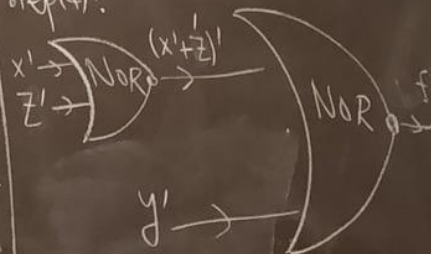


(iii) (a)

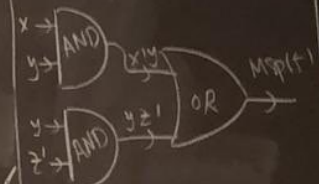

(AND-OR) circuit with 3 gates

(b)

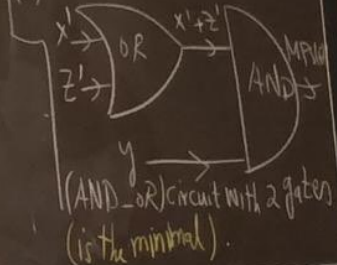

(AND-OR) circuit with 2 gates (is the minimal)

الطبعة
F.N.20
المسألة

151 Math Discrete Mathematics Boolean Algebras & Logic Gates By Malek Zein AL-Abidin

Q8. Let $f(x, y, z) = xy' + xz + y'z' + x'yz'$

- Find the Karnaugh-map for $f(x, y, z)$.
- Find $MSP(f)$ and $MPS(f)$.
- Construct a minimal circuit using (AND-OR) gates, with $f(x, y, z)$ output.
- Use NAND gates to construct circuits with $f(x, y, z)$ output.
- Use NOR gates to construct circuits with $f(x, y, z)$ output.

$MSP(f) = x'z' + xz + y'z'$
 $f' = x'z' + xyz'$
 $MPS(f) = (f')' = (x'z' + xyz')' = (x+z')(x'+y'+z)$

Karnaugh map for $f(x, y, z)$ with variables x, y, z . The map shows 1s at (0,1,0), (1,0,0), (1,0,1), and (1,1,0). The prime implicants are $x'z'$, xz , and $y'z'$.

Karnaugh map for $f'(x, y, z) = x'z' + xyz'$. The map shows 1s at (0,1,0) and (1,0,0). The prime implicants are $x'z'$ and xyz' .

#8 (a) NAND

Step(1): $MSP(f) = x'z' + xz$

Step(2): $f' =$

Step(3): $f = (f')' =$

Step(4):

#8] (a) NAND

Step(1): $Mps(f) = x'z' + xz + y'z'$

Step(2): $f' =$

Step(3): $f = (f')' =$

Step(4):


(b) NOR

Step(1): $Mps(f) = (x+z')(x+y+z)$


Step(2):

Step(3):


Step(4):

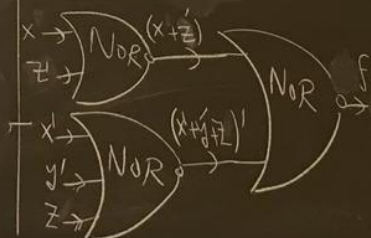

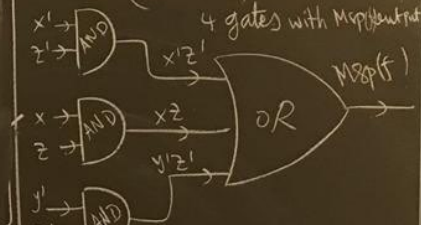(ii) (a) (AND-OR) circuit with 4 gates with Mps(f) output



(b) (AND-OR) circuit with 3 gates

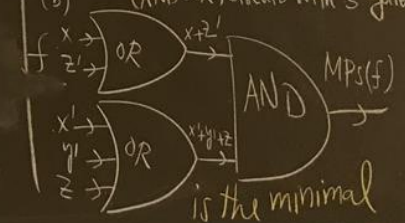

is the minimal

الحرف الرئيسي هو الجاد أقل عدد ممكن مستطيلات الأربعة

(بدون تكرار) والتي تحتوي على أكبر عدد ممكن من الحروف

المجاورة أفقياً أو عمودياً والتي كدها:

عدد الحروف
 $2^3 = 8$

$$2^2 = 4$$

$$2^1 = 2$$

$$2^0 = 1 \text{ (حالة منفردة)}$$

Q12. Let

#

	zw	z'w	z'w'	zw'
xy	0	0	0	0
xy'	0	0	0	0
x'y'	0	0	0	0
x'y	0	0	0	0

فقر با نولها 4 f

Be the Karnaugh -map for $f(x, y, z)$.

(i) Find MSP(f) and MPS(f).

(ii) Construct a minimal circuit using (AND-OR) gates, with $f(x, y, z)$ output.

(iii) Use NAND gates to construct circuits with $f(x, y, z)$ output.

(iv) Use NOR gates to construct circuits with $f(x, y, z)$ output.

$f' = x'z'w + yz'w' + yzw + x'zw'$

$Mps(f) = (f')' = (x + z + w)(y' + z + w)(y' + z' + w')(x + z' + w)$

سبحان
سبحان

	zw	zw'	$z'w'$	$z'w$
xy		1		1
xy'	1	1	1	1
$x'y'$	1		1	
$x'y$				

$$MSP(f) = y'z'w' + xz'w + xzw' + y'zw$$

Both are suitable to be minimal

Q14. Let

$MSP(f) = W' + x'y + x'yz$

	zw	zw'	z'w	z'w'
xy				
xy'				
x'y'				
x'y				

Be the Karnaugh-map for $f(x, y, z)$.

(i) Find $MSP(f)$ and $MPS(f)$.

(ii) Construct a minimal circuit using (AND-OR) gates, with $f(x, y, z)$ output.

(iii) Use NAND gates to construct circuits with $f(x, y, z)$ output.

(iv) Use NOR gates to construct circuits with $f(x, y, z)$ output.

SMARTboard

Boolean Algebra

1-

	zw	zw'	$z'w$	$z'w'$
xy				
xy'				
$x'y'$				
$x'y$				

2-

	zw	zw'	$z'w$	$z'w'$
xy				
xy'				
$x'y'$				

Windows taskbar: 1:55 PM 12/5/2018

2-

	zw	zw'	$z'w$	$z'w'$
xy	1	1		
xy'	1	1		
$x'y'$				
$x'y$	1	1		

3-

	zw	zw'	$z'w$	$z'w'$

151 Math Discrete Mathematics Boolean Algebras & Logic Gates By: Malek Zein Al-Abidin

2-


	zW	zW'	$z'W'$	$z'W$
xy			0	
xy'			0	
$x'y'$	0	0	0	0
$x'y$				0

3-

	zW	zW'	$z'W'$	$z'W$

151 Math Discrete Mathematics Boolean Algebras & Logic Gates By: Malek Zein AL-Abidin

سبحان الله وبحمده
سبحان الله العظيم

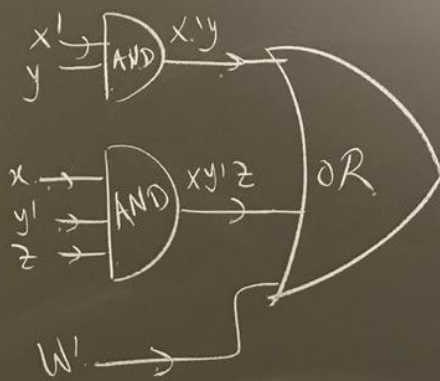

3 gates of AND-OR
is minimal

	zw	zw'	$z'w'$	$z'w$
xy		1		1
xy'	1	1	1	1
$x'y$	1		1	
$x'y'$				

$$MSp(f) = y'z'w' + xz'w + xzw' + y'zw$$

Both are suitable to be minimal

Q14. Let

	zw	z'w	z'w'	zw'
xy	1	0	0	1
xy'	0	0	0	1
x'y'	1	0	0	1
x'y	0	0	0	0

$MSP(f) = w' + x'y + x'yz$
 $f' = x'y'w + y'z'w + xyw$
 $MPS(f) = (f') = (x+y+w') \cdot (y+z+w') \cdot (x'+y'+w')$

Be the Karnaugh-map for $f(x, y, z)$.

- Find $MSP(f)$ and $MPS(f)$.
- Construct a minimal circuit using (AND-OR) gates, with $f(x, y, z)$ output.
- Use NAND gates to construct circuits with $f(x, y, z)$ output.
- Use NOR gates to construct circuits with $f(x, y, z)$ output.